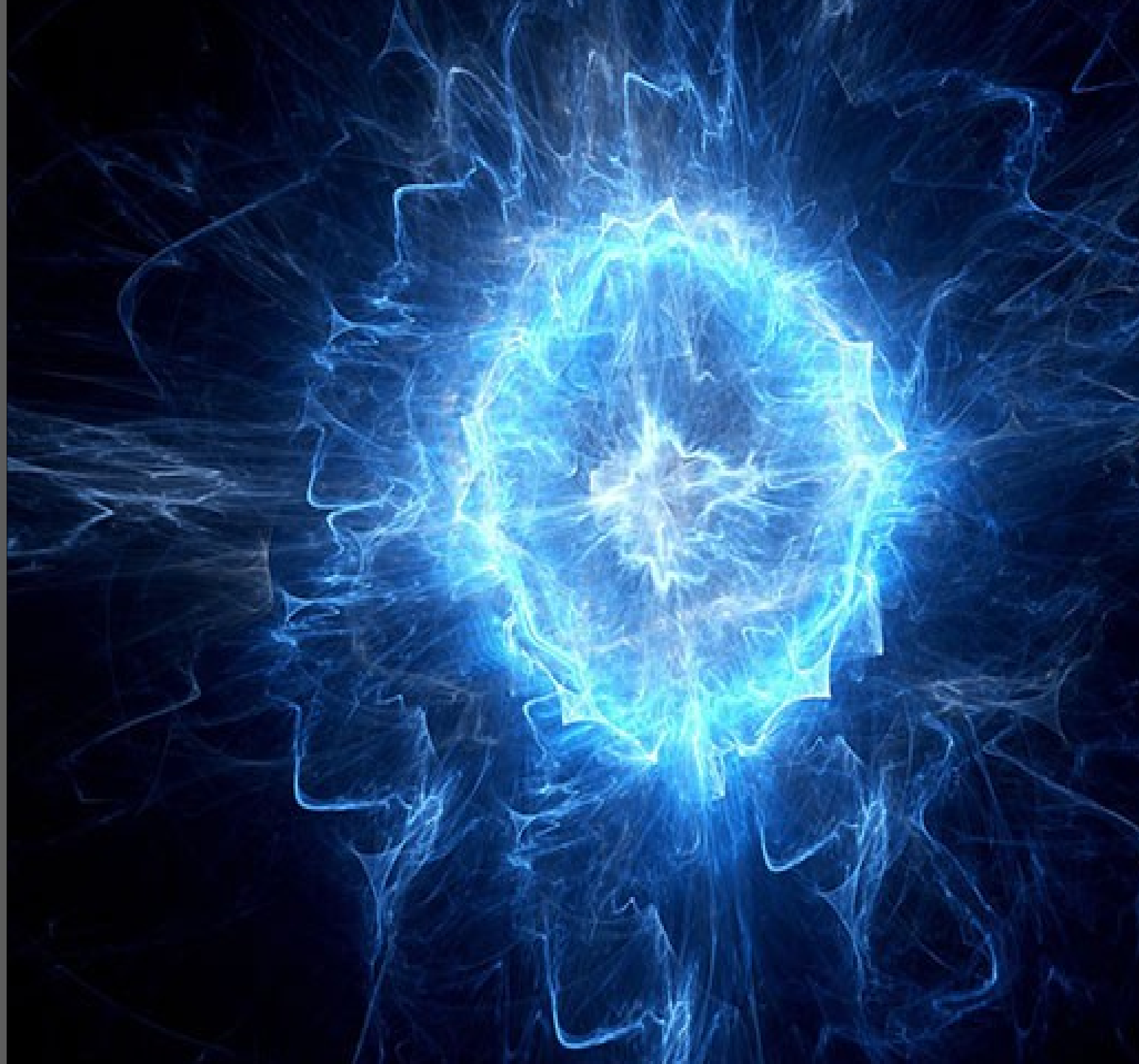


Linear DC Circuits: Basic Concepts and Analysis Using Ohm's and Kirchhoff's Laws

Lecturer Dosbayev Zh.



Contents

Introduction

Basic Concepts and Definitions

Direct Current (DC) Electric Charge, Current, Voltage, and Resistance

Ohm's Law

Kirchhoff's Laws

Kirchhoff's Current Law (KCL)

Kirchhoff's Voltage Law (KVL)


Application of Ohm's and Kirchhoff's Laws

Steps for Analyzing DC Circuits

Potential Diagrams

Conclusion

References

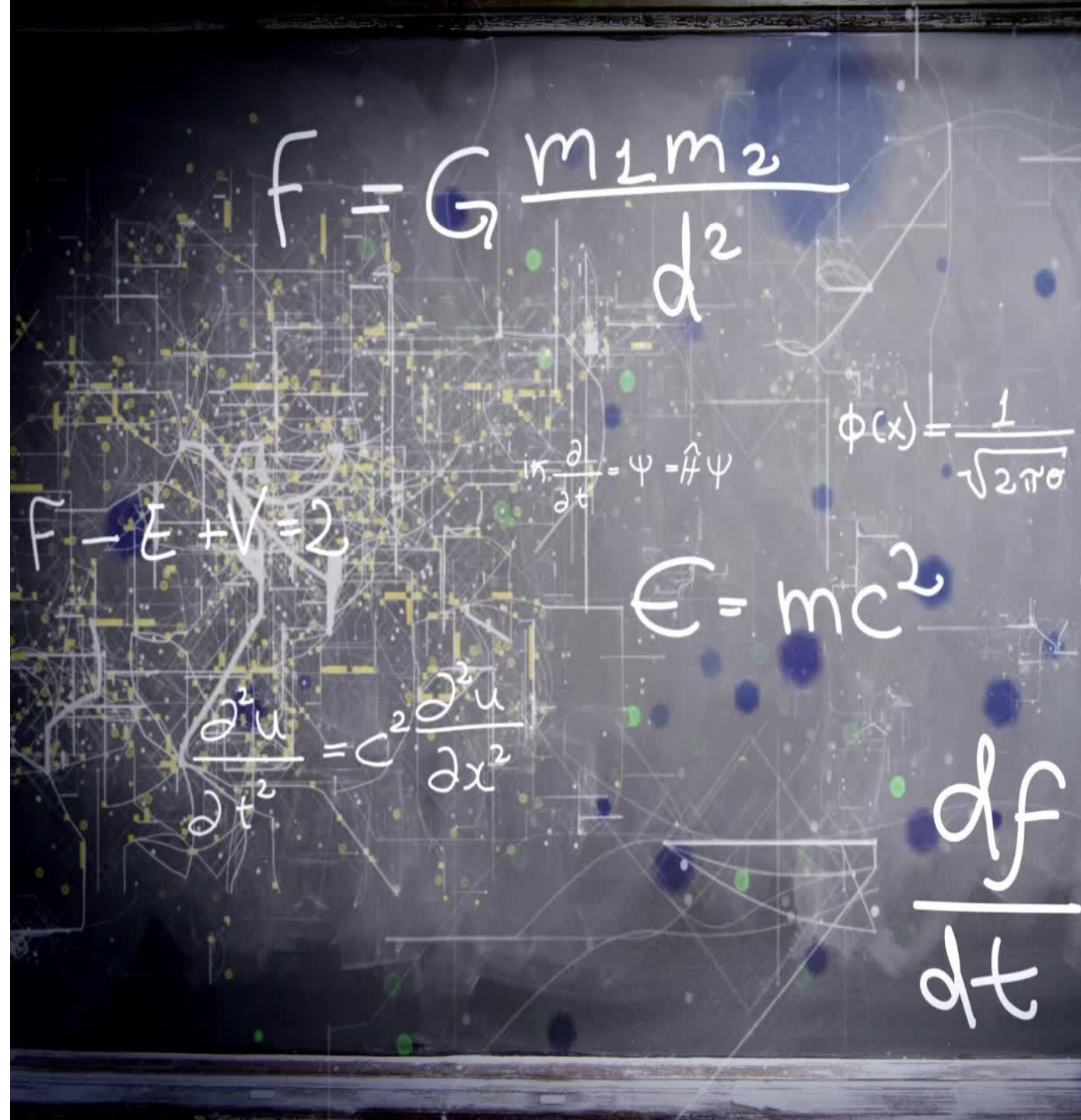




Abstract

This presentation provides an overview of the fundamental concepts of linear DC circuits, including Ohm's Law and Kirchhoff's Laws, which form the foundation for electrical circuit analysis. We will explore how these laws are applied in calculating current, voltage, and resistance in simple and complex electrical circuits. Potential diagrams are also introduced as a tool to visualize voltage distribution across circuit components.

Basic Concepts and Definitions

- **Direct Current (DC):** The flow of electric charge in a single direction, commonly found in batteries and some power supplies.
- **Electric Charge (Q):** The property of particles that causes them to experience a force when in an electric field, measured in Coulombs (C).
- **Electric Current (I):** The rate of flow of charge through a conductor, measured in Amperes (A).
- **Voltage (V):** The potential difference between two points, measured in Volts (V).
- **Resistance (R):** The opposition to current flow, measured in Ohms (Ω).



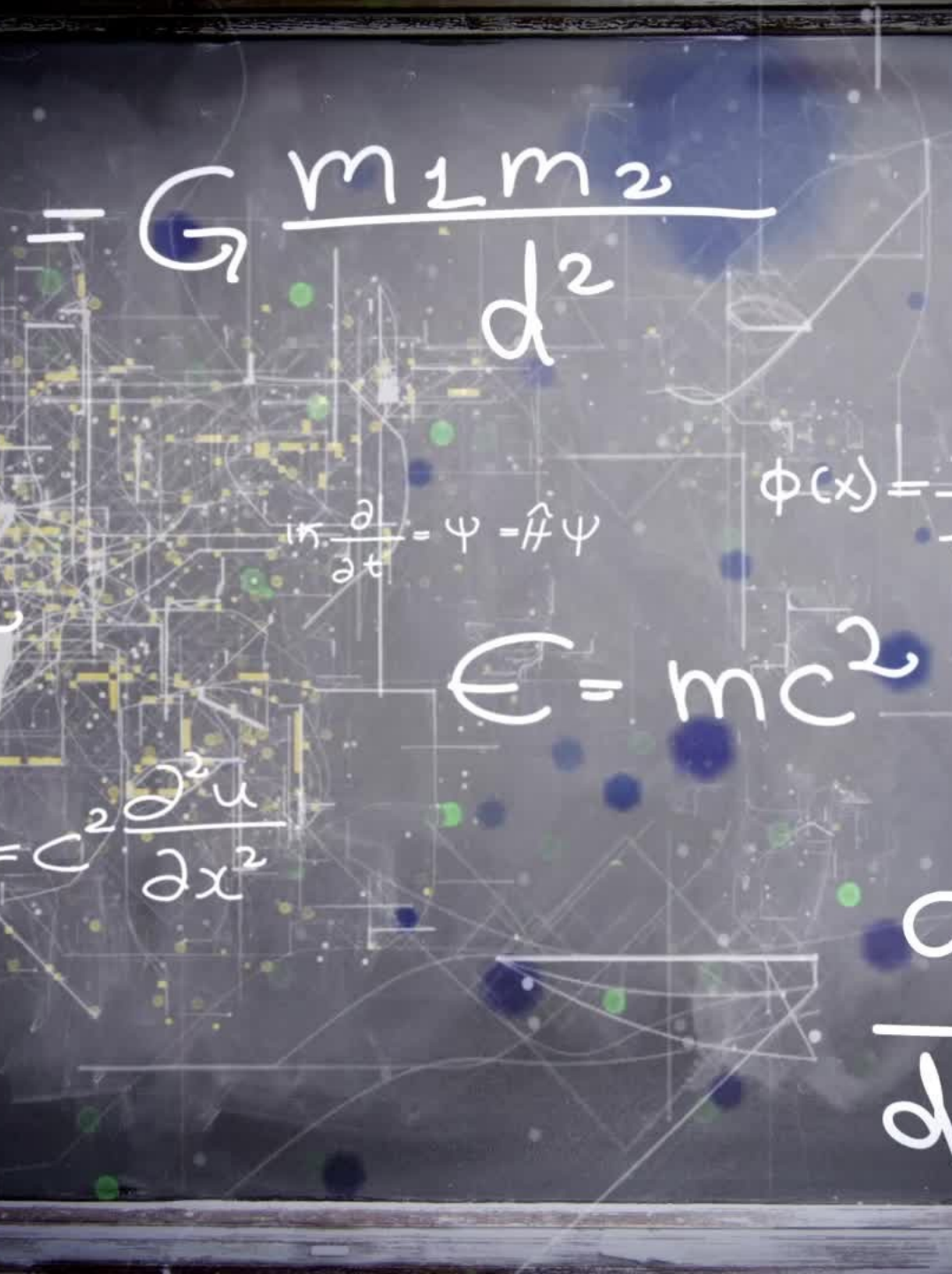

Ohm's Law


- **Formula:** $V=IR$
- Ohm's Law describes the linear relationship between voltage (V), current (I), and resistance (R) in an electrical circuit.
- Example calculation to demonstrate using Ohm's Law in a basic circuit.




Kirchhoff's Laws

- **Kirchhoff's Current Law (KCL):** The total current entering a junction equals the total current leaving it, ensuring current conservation.
- **Kirchhoff's Voltage Law (KVL):** The sum of the voltages around any closed loop in a circuit must equal zero, maintaining energy conservation.

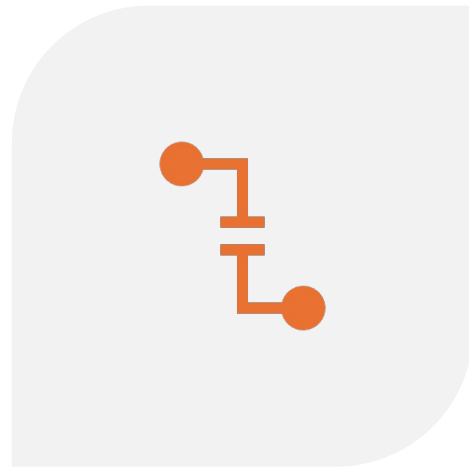
Application of Ohm's and Kirchhoff's Laws



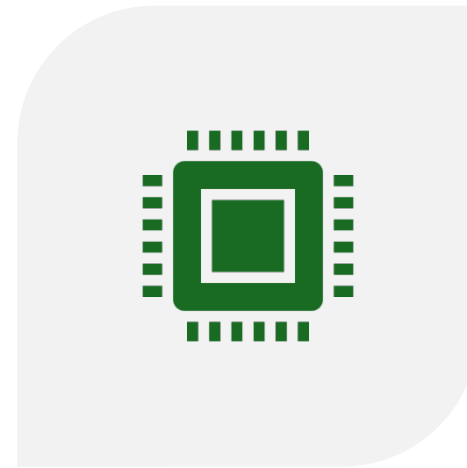ANALYZING SIMPLE CIRCUITS: USE OHM'S LAW FOR SERIES AND PARALLEL CIRCUITS TO DETERMINE VOLTAGE AND CURRENT.



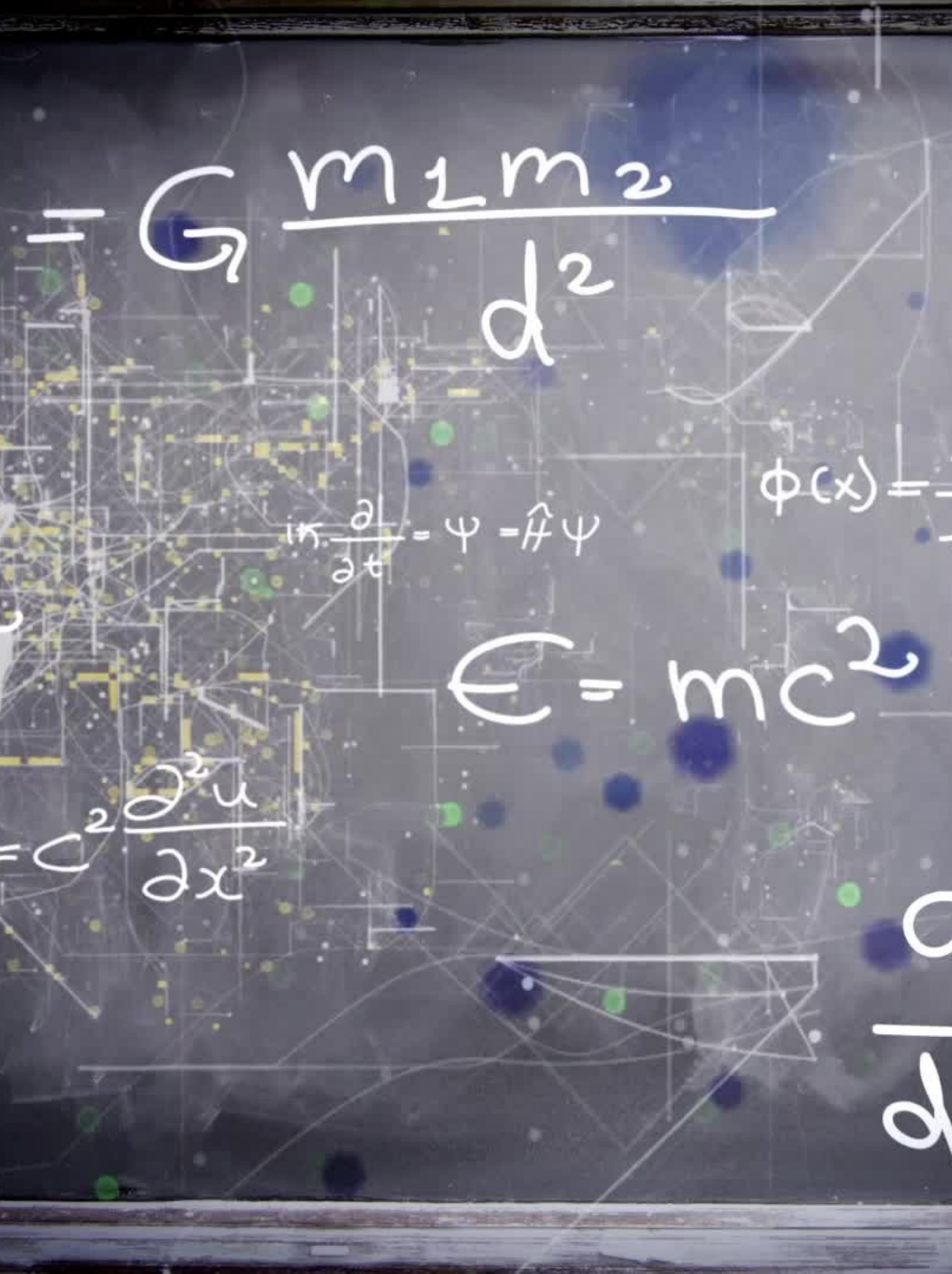ANALYZING COMPLEX CIRCUITS: APPLY KIRCHHOFF'S LAWS TO SOLVE FOR UNKNOWN IN CIRCUITS WITH MULTIPLE BRANCHES AND LOOPS.




Potential Diagrams

- **Definition:** Graphical representations that show voltage changes across each element in the circuit.
- **Use:** Helps to visualize potential drops and gains, aiding in the understanding of KVL in circuits.

Conclusion

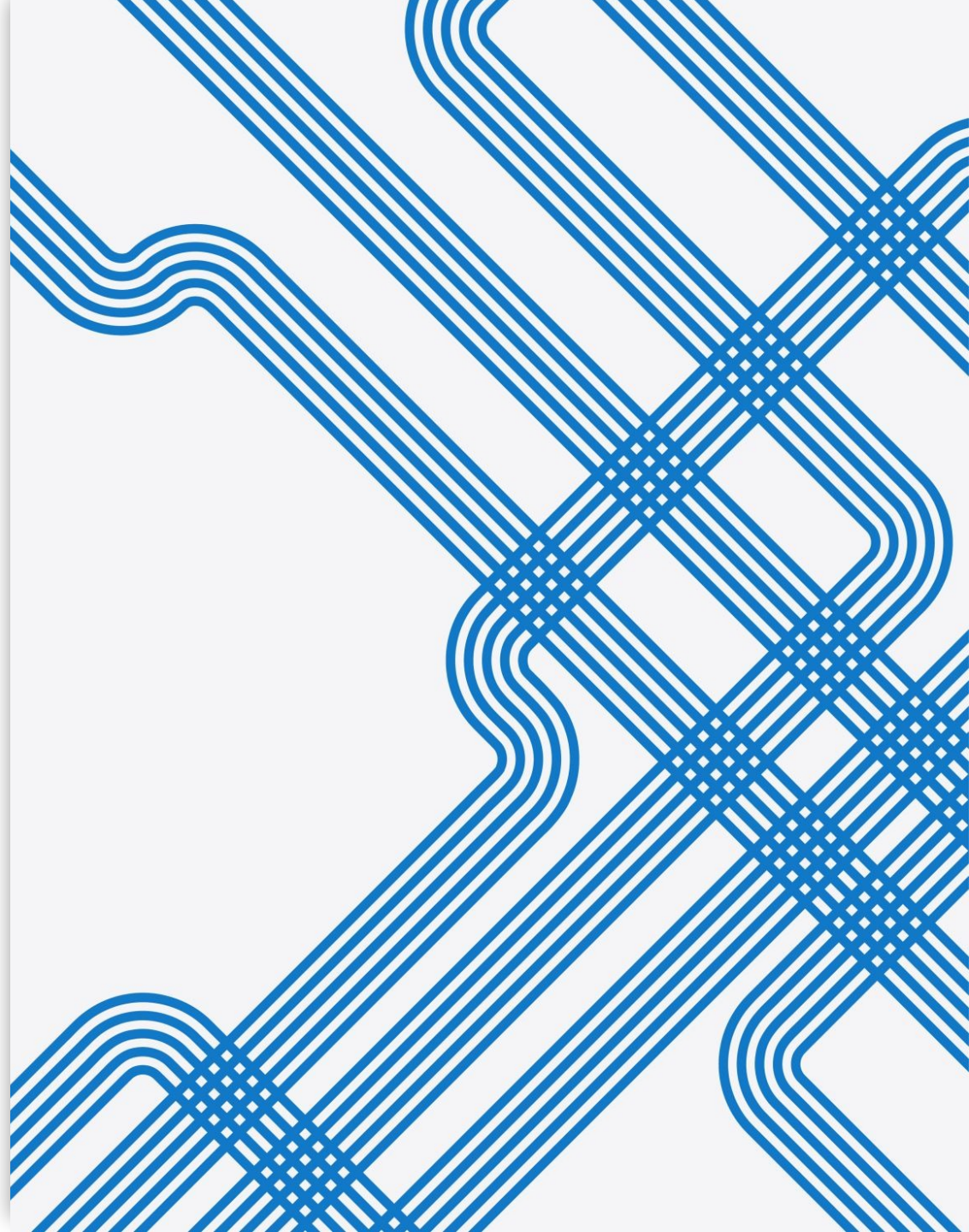Understanding the basic concepts and principles, such as Ohm's Law and Kirchhoff's Laws, is essential for analyzing linear DC circuits. By mastering these tools, we can accurately calculate current, voltage, and resistance, and utilize potential diagrams for clearer insights into voltage distribution.



References

1. Alexander, C. K., & Sadiku, M. N. O. "Fundamentals of Electric Circuits." – 2021.
2. Hayt, W., & Kemmerly, J. "Engineering Circuit Analysis." – 2019.
3. Dorf, R. C., & Svoboda, J. A. "Introduction to Electric Circuits." – 2020.
4. Boylestad, R. L. "Introductory Circuit Analysis." – 2018.