

СӘТБАЕВ
УНИВЕРСИТЕТИ



SATBAYEV
UNIVERSITY


Lecture 12

Three-Phase Load Calculations: Star (Wye) and Delta Configurations

Senior lecturer: Dosbayev Zh.M.

Introduction to Three-Phase Electrical Systems

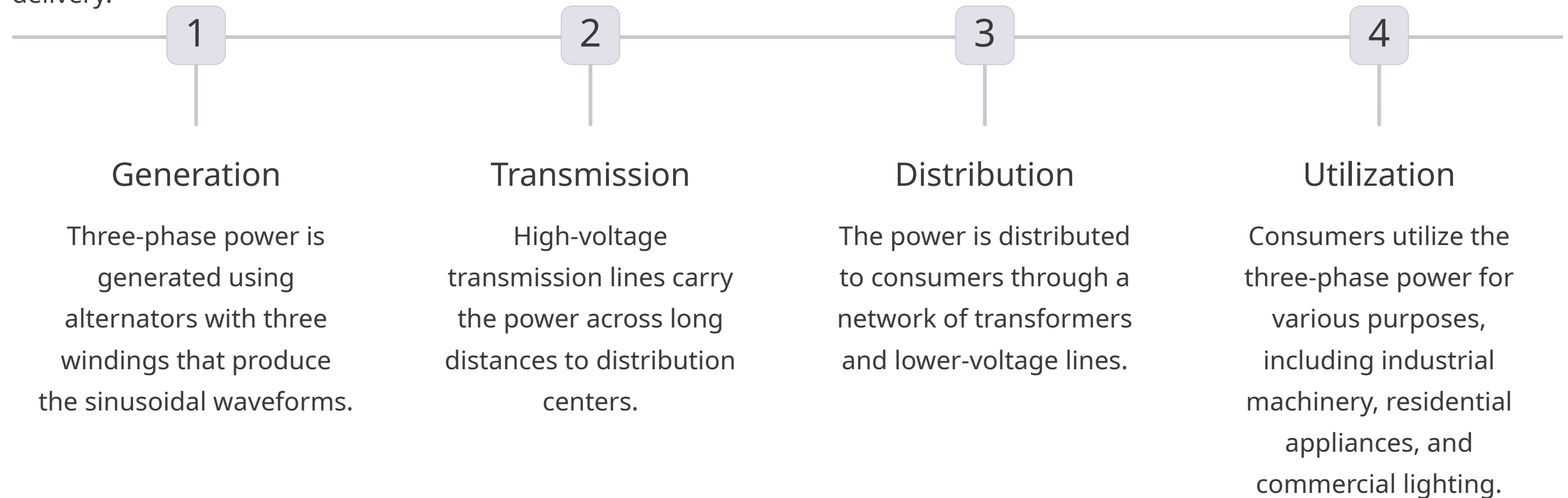Three-phase systems offer significant advantages over single-phase systems, including improved efficiency, reduced voltage fluctuations, and the ability to deliver higher power. The three phases are typically represented as A, B, and C, each carrying an alternating current that is 120 degrees out of phase with the others. This phase shift ensures a smooth and continuous power delivery.



Review of Star (Wye) and Delta Configurations

Three-phase loads can be connected in two primary configurations: star (wye) and delta. In a star configuration, the ends of each phase winding are connected to a common neutral point, creating a "Y" shape. In a delta configuration, the windings are connected end-to-end, forming a triangle. The choice of configuration depends on factors like voltage requirements, load balance, and system efficiency.

Star (Wye)

Wye configuration offers a neutral point for grounding and fault protection. It's suitable for high-voltage applications and unbalanced loads.

Delta

Delta configuration is commonly used for high-power applications and balanced loads. It's simpler to connect but doesn't have a neutral point.

Assumptions and Prerequisites

To accurately calculate three-phase loads, certain assumptions and prerequisites need to be understood. These include:

1 Balanced Load

The assumption of a balanced load means that all three phases have equal impedance and draw the same amount of current.

3 Line-to-Line Voltage

We use the line-to-line voltage (VLL), which is the voltage between any two phases. The line-to-neutral voltage (VLN) is also important for calculations.

2 Sinusoidal Waveforms

We assume the voltage and current waveforms are sinusoidal, which is typical in AC power systems.

4 Power Factor

The power factor (PF) represents the phase difference between voltage and current, impacting the efficiency of power delivery.




Calculating Wye-Connected Load Parameters

In a wye configuration, the line-to-line voltage (V_{LL}) is $\sqrt{3}$ times greater than the line-to-neutral voltage (V_{LN}). To calculate load parameters like current and power, we use the following formulas:

Line Current (I_L)	$I_L = I_{ph} = V_{LN} / Z_{ph}$
Phase Current (I_{ph})	Same as Line Current
Phase Voltage (V_{ph})	$V_{ph} = V_{LN}$
Total Power (P_T)	$P_T = 3 * V_{ph} * I_{ph} * PF$

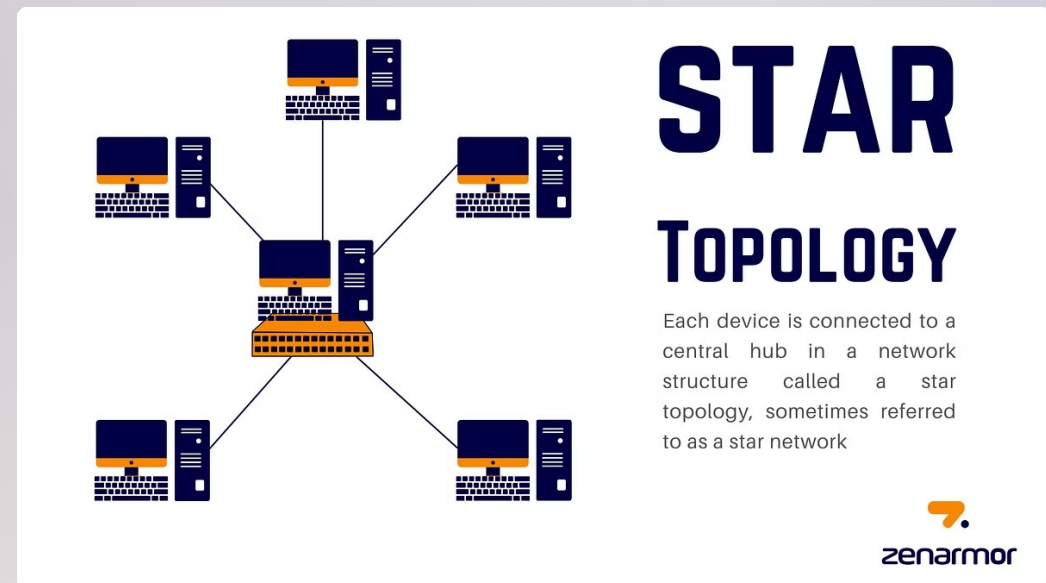Where Z_{ph} is the impedance of each phase winding and PF is the power factor.



Calculating Delta-Connected Load Parameters

In a delta configuration, the line-to-line voltage (VLL) is equal to the phase voltage (Vph). The line current (IL) is $\sqrt{3}$ times greater than the phase current (Iph). The formulas for calculating load parameters are as follows:

Ohm's Law: $E_p = I_p Z_p$

Real Power: $P = 3 E_p I_p PF$ $P = \sqrt{3} E_L I_L PF$


Apparent Power: $S = \sqrt{P^2 + Q^2}$ $S = 3 E_p I_p$ $S = \sqrt{3} E_L I_L$

Reactive Power: $Q = \sqrt{S^2 - P^2}$

Power Factor: $PF = \frac{P}{S}$

Line Current (IL)	$IL = \sqrt{3} * I_{ph}$
Phase Current (Iph)	$I_{ph} = V_{ph} / Z_{ph}$
Phase Voltage (Vph)	$V_{ph} = V_{LL}$
Total Power (PT)	$PT = 3 * V_{ph} * I_{ph} * PF$

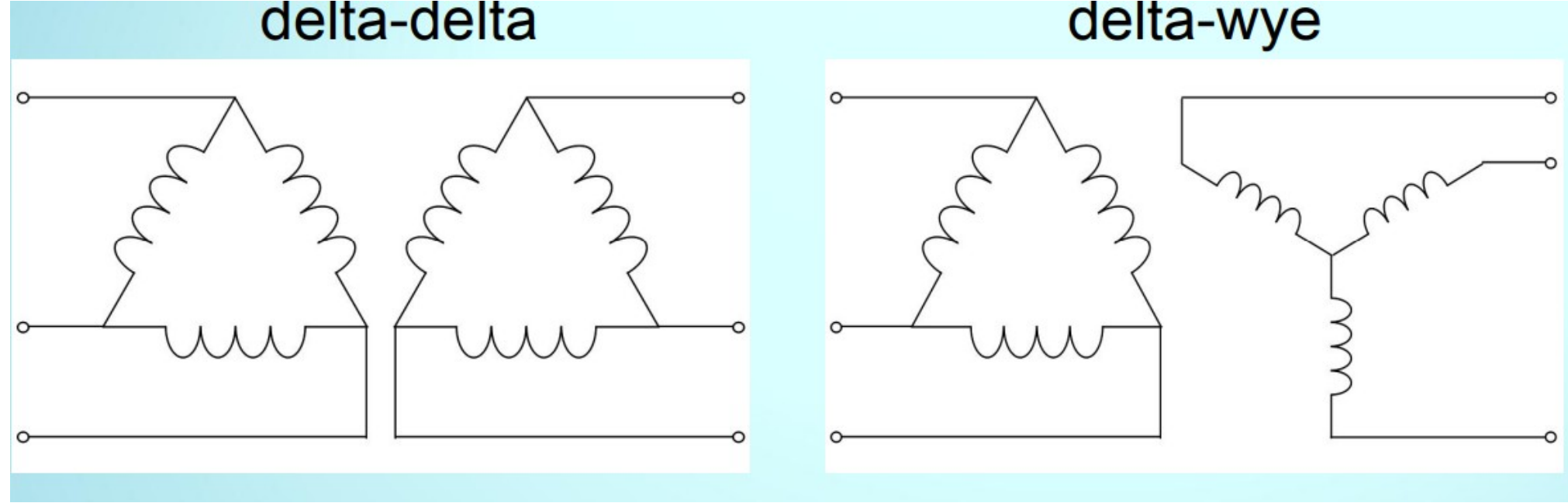Remember that Zph is the impedance of each phase winding, and PF is the power factor.



Comparison of Wye and Delta Configurations

Comparing wye and delta configurations highlights their unique characteristics and applications:

	Wye	Delta
Neutral Point	Present	Absent
Voltage Relationship	$V_{LL} = \sqrt{3} * V_{LN}$	$V_{LL} = V_{ph}$
Current Relationship	$I_L = I_{ph}$	$I_L = \sqrt{3} * I_{ph}$
Application	High-voltage, unbalanced loads	High-power, balanced loads

Practical Considerations and Applications

Understanding the practical implications of different load configurations is vital for real-world applications. These considerations include:

1 Load Balancing

Maintaining a balanced load across all three phases is crucial for efficient operation and minimizing voltage fluctuations.

3 Grounding

Proper grounding in wye configurations ensures safety and protects against electrical faults.

2 Power Factor Correction

Improving the power factor by using capacitors or other methods reduces energy losses and improves the overall efficiency of the system.

4 Fault Protection

Fuses and circuit breakers are essential for protecting the system from short circuits and overloads.



Load Balancing and Power Factor Correction

Load balancing is critical in three-phase systems to ensure each phase carries an equal share of the load. Unbalanced loads can lead to voltage imbalances and inefficient power distribution. Power factor correction aims to improve the efficiency of the system by reducing the phase difference between voltage and current. This is typically achieved by installing capacitor banks in parallel with the load.

1

Load Balancing

Distributing the load equally among the three phases to minimize voltage imbalances.

2

Power Factor Correction

Improving the power factor by using capacitors to reduce the phase angle between voltage and current.

3

System Efficiency

Reducing energy losses and improving the overall efficiency of power delivery.



Conclusion and Key Takeaways

Calculating three-phase loads in star and delta configurations is a fundamental aspect of electrical system design and analysis. Understanding the different connections, voltage and current relationships, and practical considerations is essential for engineers, technicians, and anyone working with three-phase power systems. By mastering these concepts, you can ensure efficient, reliable, and safe power distribution for various applications.



Star (Wye)

Offers a neutral point, suitable for high-voltage and unbalanced loads.



Delta

No neutral point, commonly used for high-power and balanced loads.




Load Balancing

Ensures equal load distribution across all phases for efficient operation.



Power Factor Correction

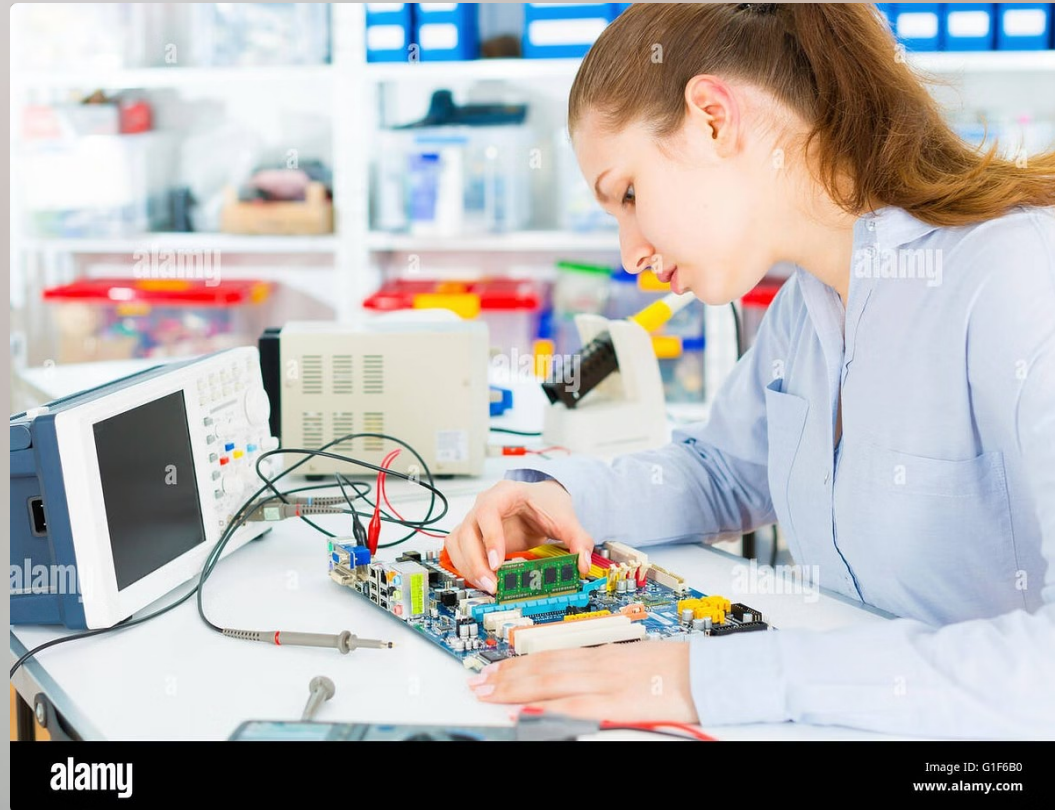Improves system efficiency by reducing the phase angle between voltage and current.



List of references

1. Wadhwa, C.L. Electrical Power Systems. A foundational text on three-phase systems, covering star and delta configurations.
2. Glover, J. Duncan, and Sarma, Mulukutla S. Power System Analysis and Design. Provides key insights into power system concepts and load calculations.
3. Kirtley Jr., James L. Electric Power Principles. Practical explanations of three-phase systems with real-world examples.
4. IEEE Xplore and ScienceDirect - Research articles on three-phase load calculations and power systems.
5. MIT OpenCourseWare - Lecture notes on three-phase power, with exercises and detailed explanations.